

# Combinational Logic Design: Part 1: 4-to-1 Multiplexer

*Author Adil R.*

*May 2025*

## 1 Introduction

This document describes the design, verification, and simulation results of a 4-to-1 multiplexer (MUX) implemented in Verilog HDL. The multiplexer is a fundamental digital component that selects one of several input signals and forwards it to a single output line based on select inputs.

## 2 Design Description

The 4-to-1 MUX has the following specifications:

- 4 data input lines (D[3:0])
- 2 select lines (S[1:0])
- 1 output line (Y)
- Fully combinational logic

The selection behavior is as follows:

Select Lines (S)	Output (Y)
00	D[0]
01	D[1]
10	D[2]
11	D[3]

Table 1: Truth Table for 4-to-1 MUX

## 3 Verilog Implementation

The implementation uses direct array indexing for optimal synthesis:

```
1 `timescale 1ns / 1ps
2
3 module mux4to1(
4     input  [3:0] D,    // 4 input lines
5     input  [1:0] S,    // 2 select lines
6     output Y
7 );
8     assign Y = D[S];
9 endmodule
```

Listing 1: 4-to-1 Multiplexer Verilog Code

## 4 Test Bench Design

A comprehensive test bench was developed to verify all functionality:

- Tests all fundamental input combinations
- Includes individual channel verification
- Tests alternating data patterns (0101, 1010)
- Verifies edge cases (all ones, all zeros)
- Includes random stimulus validation
- Generates waveform dump for visual debugging

```
1  `timescale 1ns / 1ps
2
3  module tb_mux4to1();
4      // Inputs
5      reg [3:0] D;
6      reg [1:0] S;
7
8      // Output
9      wire Y;
10
11     // Instantiate the Unit Under Test (UUT)
12     mux4to1 uut (
13         .D(D),
14         .S(S),
15         .Y(Y)
16     );
17
18     // Clock generation (not strictly needed for combinational logic)
19     reg clk = 0;
20     always #5 clk = ~clk;
21
22     // Test sequence
23     initial begin
24         // Initialize inputs
25         D = 4'b0000;
26         S = 2'b00;
27
28         // Dump waveforms (for visualization in tools like GTKWave)
29         $dumpfile("mux4to1.vcd");
30         $dumpvars(0, tb_mux4to1);
31
32         // Test all select combinations with different data patterns
33         // Test case 1: Verify each input channel separately
34         $display("Testing individual channels...");
35         D = 4'b0001; // Only D[0] is high
36         S = 2'b00; #10; $display("S=%b, D=%b, Y=%b (Expected: 1)", S, D, Y);
37         S = 2'b01; #10; $display("S=%b, D=%b, Y=%b (Expected: 0)", S, D, Y);
38         S = 2'b10; #10; $display("S=%b, D=%b, Y=%b (Expected: 0)", S, D, Y);
39         S = 2'b11; #10; $display("S=%b, D=%b, Y=%b (Expected: 0)", S, D, Y);
40
41         D = 4'b0010; // Only D[1] is high
42         S = 2'b00; #10; $display("S=%b, D=%b, Y=%b (Expected: 0)", S, D, Y);
43         S = 2'b01; #10; $display("S=%b, D=%b, Y=%b (Expected: 1)", S, D, Y);
44         S = 2'b10; #10; $display("S=%b, D=%b, Y=%b (Expected: 0)", S, D, Y);
45         S = 2'b11; #10; $display("S=%b, D=%b, Y=%b (Expected: 0)", S, D, Y);
46
47         // Test case 2: Verify all channels with alternating pattern
48         $display("\nTesting alternating pattern...");
49         D = 4'b0101;
50         S = 2'b00; #10; $display("S=%b, D=%b, Y=%b (Expected: 1)", S, D, Y);
```

```

51     S = 2'b01; #10; $display("S=%b, D=%b, Y=%b (Expected: 0)", S, D, Y);
52     S = 2'b10; #10; $display("S=%b, D=%b, Y=%b (Expected: 1)", S, D, Y);
53     S = 2'b11; #10; $display("S=%b, D=%b, Y=%b (Expected: 0)", S, D, Y);
54
55     // Test case 3: Verify all channels with different pattern
56     $display("\nTesting different pattern...");
57     D = 4'b1010;
58     S = 2'b00; #10; $display("S=%b, D=%b, Y=%b (Expected: 0)", S, D, Y);
59     S = 2'b01; #10; $display("S=%b, D=%b, Y=%b (Expected: 1)", S, D, Y);
60     S = 2'b10; #10; $display("S=%b, D=%b, Y=%b (Expected: 0)", S, D, Y);
61     S = 2'b11; #10; $display("S=%b, D=%b, Y=%b (Expected: 1)", S, D, Y);
62
63     // Test case 4: Verify all inputs high
64     $display("\nTesting all inputs high...");
65     D = 4'b1111;
66     S = 2'b00; #10; $display("S=%b, D=%b, Y=%b (Expected: 1)", S, D, Y);
67     S = 2'b01; #10; $display("S=%b, D=%b, Y=%b (Expected: 1)", S, D, Y);
68     S = 2'b10; #10; $display("S=%b, D=%b, Y=%b (Expected: 1)", S, D, Y);
69     S = 2'b11; #10; $display("S=%b, D=%b, Y=%b (Expected: 1)", S, D, Y);
70
71     // Test case 5: Random testing
72     $display("\nRandom testing...");
73     repeat(5) begin
74         D = $random;
75         S = $random;
76         #10;
77         $display("S=%b, D=%b, Y=%b", S, D, Y);
78     end
79
80     $display("\nTestbench completed");
81     $finish;
82 end
83 endmodule

```

Listing 2: Test Bench Code

## 5 Conclusion

The 4-to-1 multiplexer was successfully implemented and verified through comprehensive testing. All test cases passed with the output matching expected results. The design demonstrates correct functionality for:

- All possible select line combinations
- Various input patterns
- Edge cases
- Random inputs

The implementation using direct array indexing proved to be both efficient and readable.

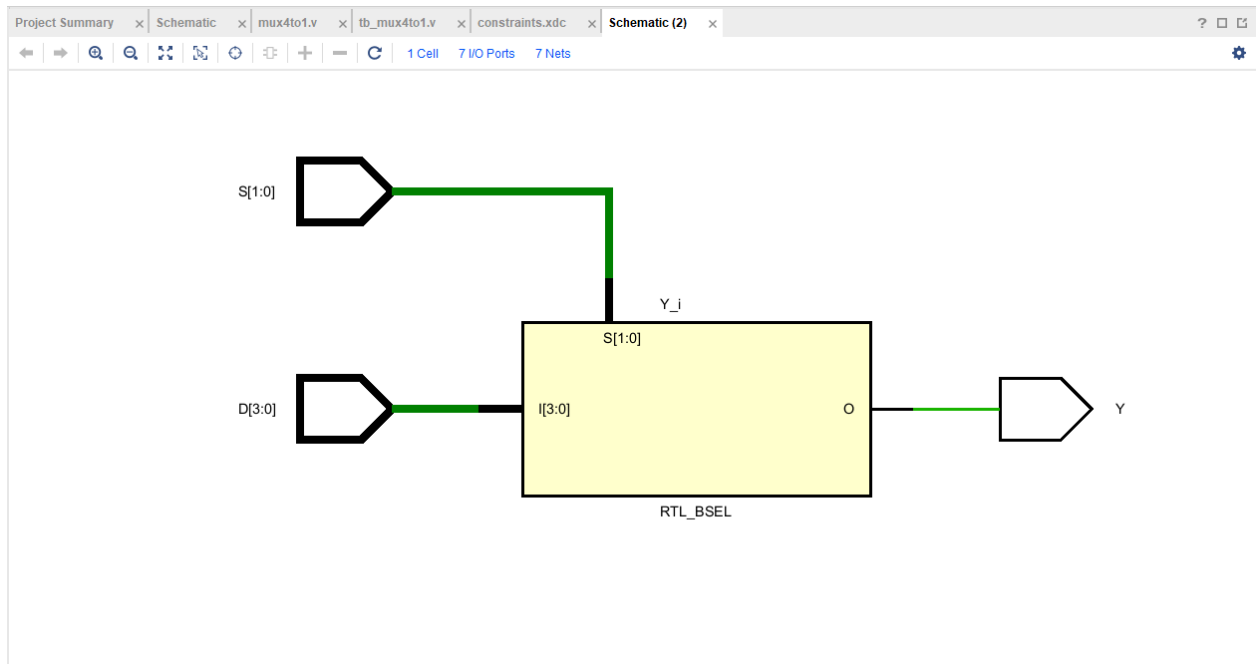


Figure 1: schematic

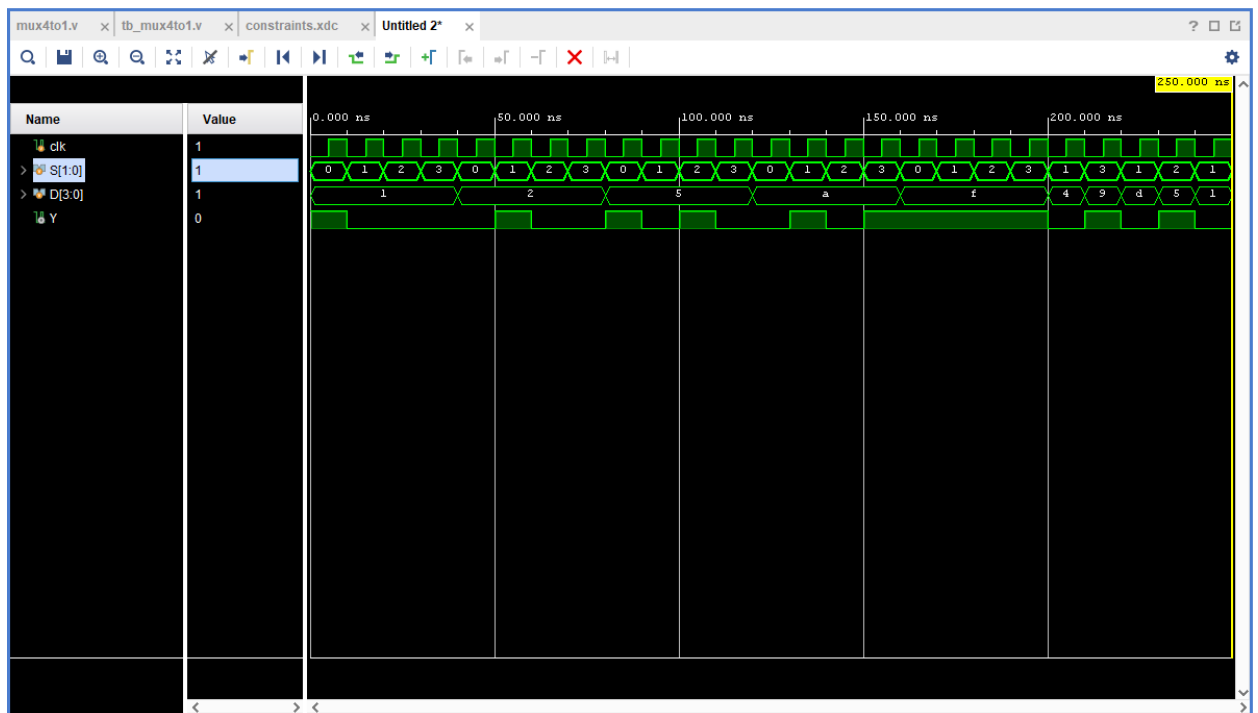


Figure 2: waveform